 


The Shell CPU

Component implementation and testing



Jonathan Rice Shelley II

October 21, 2020

Version 1.0

1 Contents

1. Component Implementation and Testing Overview
2. Control Unit Verification
3. Component Testing

2 Component Implementation and Testing Overview

This document details the implementation and testing of each unique component in the Shell CPU. The VHDL for each module is too long to be listed in this document and can be found [here](#) link.

3 Control Unit Verification

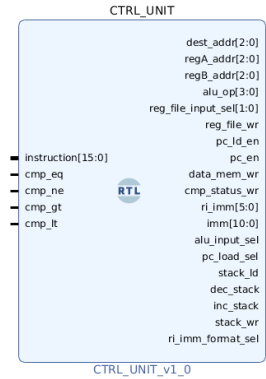


Figure 1: CPU Control Unit

The control unit is tested against all 23 instructions in the Shell ISA. The order of the instructions tested can be seen in the table below. The control unit output to the instructions is shown in Figure 2.

Instruction test order
hlt
add r1, r2, r3
sub r1, r2, r3
and r2, r2, r3
or r1, r2, r3
xor r1, r2, r3
nand r1, r2, r3
lw r1, r2
sw r1, r2
asr r1, r2
asl r1, r2
cmp r1, r2
jalr r1, r2
push r1
pop r1
lsp r1
addi r1, 5
subi r1, 5
lui r1, 5
beq 5
bne 5
bgt 5
blt 5

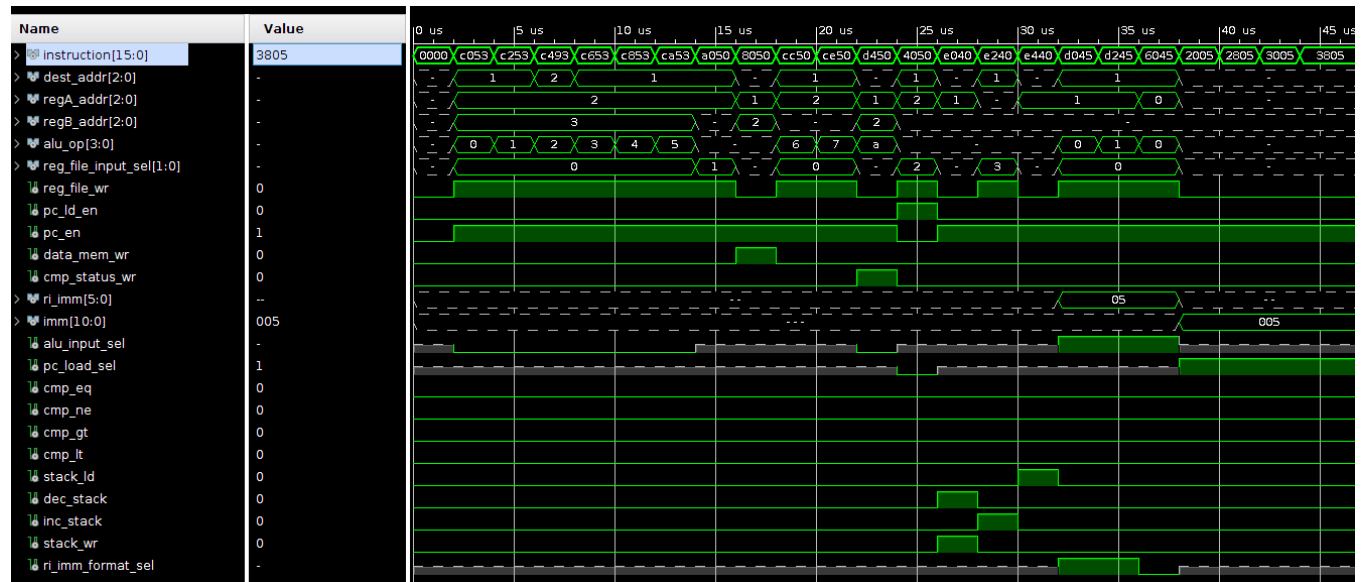


Figure 2: CPU Control Testbench

The outputs of the simulated control unit have been verified with the expected values listed in the Shell datapath documentation.

4 Component Testing

4.1 Arithmetic Logic Unit

 


Figure 3: Arithmetic Logic Unit

HDL and Verification

The arithmetic logic unit or ALU performs arithmetic operations on data in the CPU. The block is entirely combinational logic and controlled by its "op" signals. A testbench is created to verify the functionality of the ALU. Figure 4 shows the ALU undertest performing each operation.

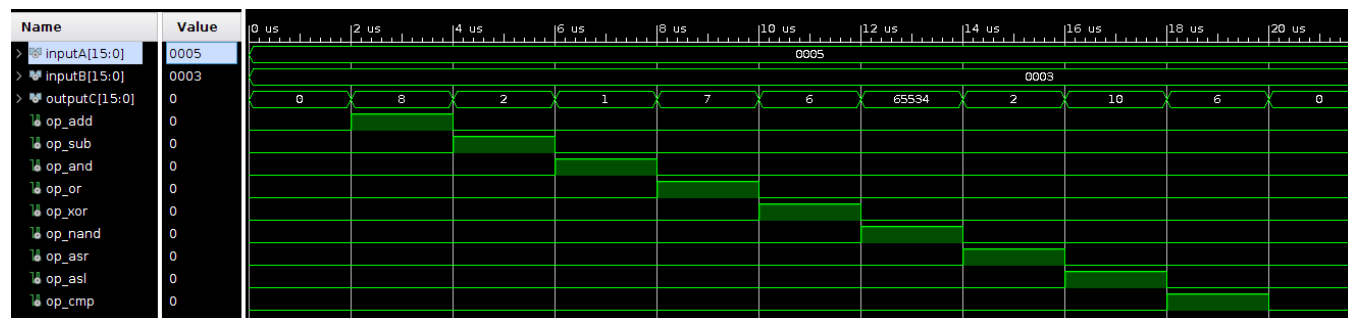


Figure 4: Arithmetic Logic Unit

4.2 Simple Adder

 


Figure 5: Simple Adder Unit

HDL and Verification

The simple adder block is used to sum values together within the CPU datapath. The block is used once to calculate $PC + 1$. The block is used a second time to find $pc + imm$ for B-Type instructions. The testbench results for the simple adder can be seen in Figure 6. From the testbench it can be concluded that the simple adder properly adds the two decimal numbers.

 


Figure 6: Simple Adder Unit Testbench

4.3 Arithmetic Logic Unit Controller

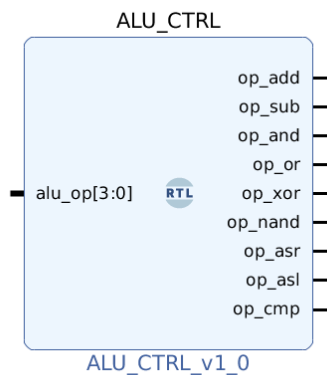


Figure 7: Arithmetic Logic Unit Controller

HDL and Verification

The arithmetic logic unit controller is used to interpret the ALU op codes from the CPU controller. The outputs of the arithmetic logic unit controller directly control what operation the ALU performs. The ALU control unit can be seen correctly decoding `alu_op` in Figure 8.

 


Figure 8: Arithmetic Logic Unit Controller Testbench Results

4.4 Two to One Multiplexer



Figure 9: Two to One Multiplexer

HDL and Verification

The two to one multiplexer is used throughout the datapath to mux 16-bit buses. The functionality of the mux is verified as seen in Figure 10.

 


Figure 10: Two to One Multiplexer Testbench

4.5 Comparator Status Register



Figure 11: Comparator Status Register

HDL and Verification

The comparator status register stores the results of a comparison. The testbench for this component can be seen in Figure 12.

 


Figure 12: Comparator Status Register Testbench

4.6 11-bit Immediate Sign Extend

 


Figure 13: 11-bit Immediate Sign Extend

HDL and Verification

Used to sign extend 11-bit immediates from B-type instructions. Verification of this component can be seen in Figure 14.

 


Figure 14: 11-bit Immediate Sign Extend Testbench

4.7 Program Counter Register

 


Figure 15: Program Counter Register

HDL and Verification

Program counter used to keep the address of the next instruction in memory. Verification of the program counter can be seen in Figure 16.

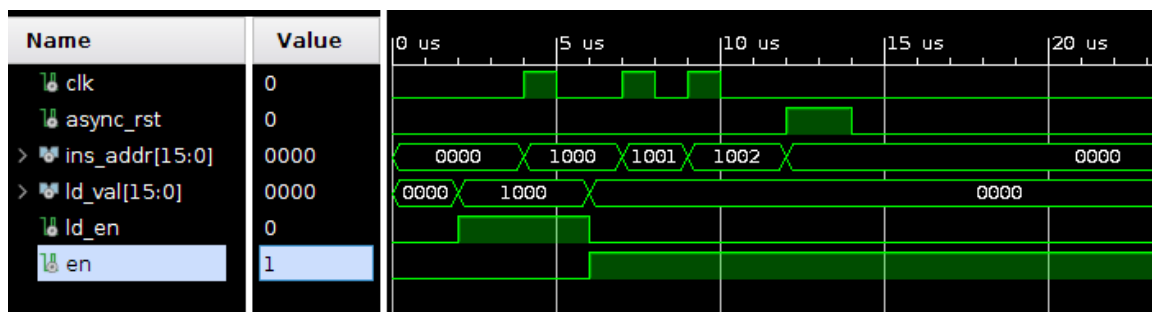


Figure 16: Program Counter Register Testbench

4.8 General Purpose Register File

 


Figure 17: General Purpose Register File

HDL and Verification

GPR (General Purpose Register) file is used to store temporary values during computation. The verification of the register file can be seen in Figure 18.

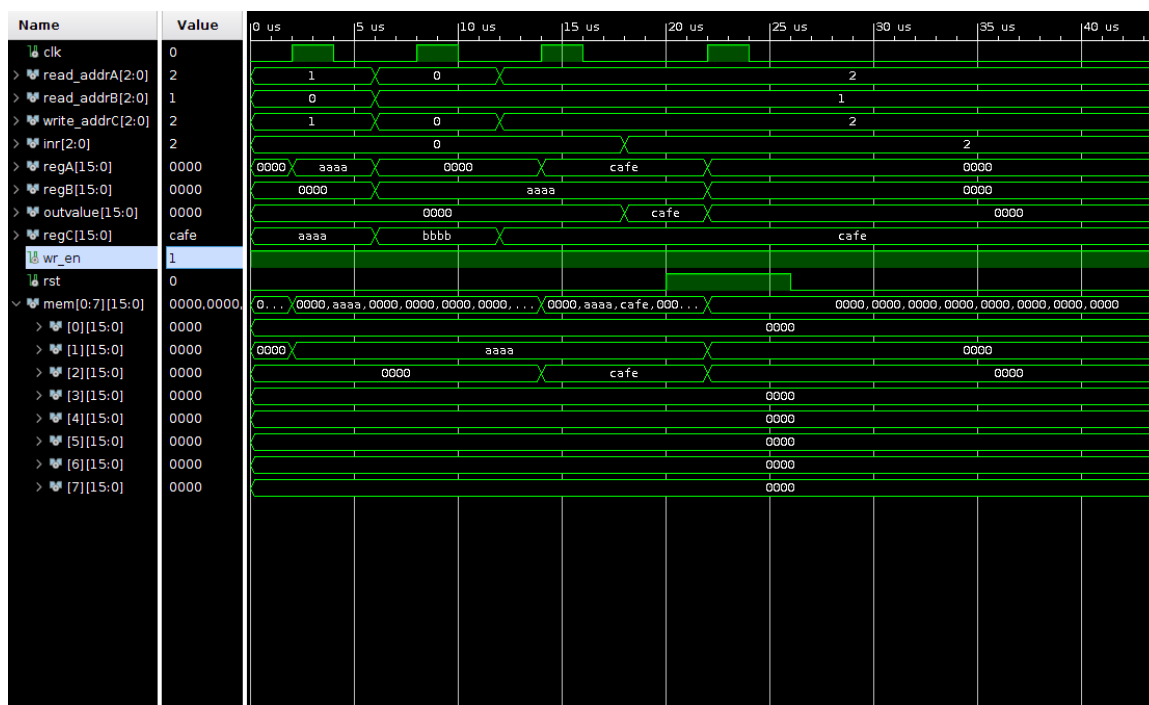


Figure 18: General Purpose Register File

4.9 Register File Input Multiplexer

 


Figure 19: Register File Input Multiplexer

HDL and Verification

Used to multiplex the data input to the GPR file. The verification of this component can be seen in Figure 20.

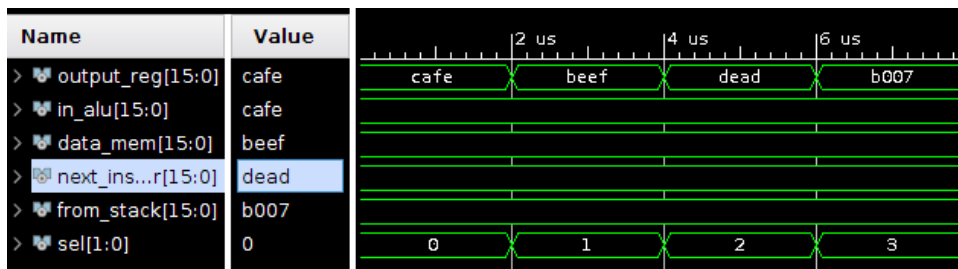


Figure 20: Register File Input Multiplexer

4.10 RI-Type Zero Extend Immediate & RI-Type Immediate Upper 6-bit Concatenation

 


Figure 21: RI-Type Zero Extend Immediate

 


Figure 22: RI-Type Immediate Upper 6-bit Concatenation

HDL and Verification

The immediate zero extend module and immediate upper 6-bit concatenation module are verified below in Figure 23.

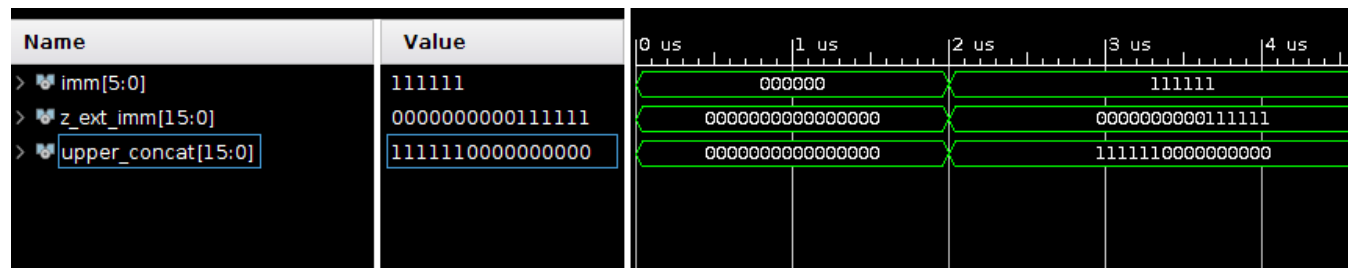


Figure 23: RI-Type Zero Extend Immediate

4.11 Stack Pointer Register

 


Figure 24: Stack Pointer Register

HDL and Verification

Stack pointer register maintains stack pointer. Verification of the stack pointer module can be seen in Figure 25.

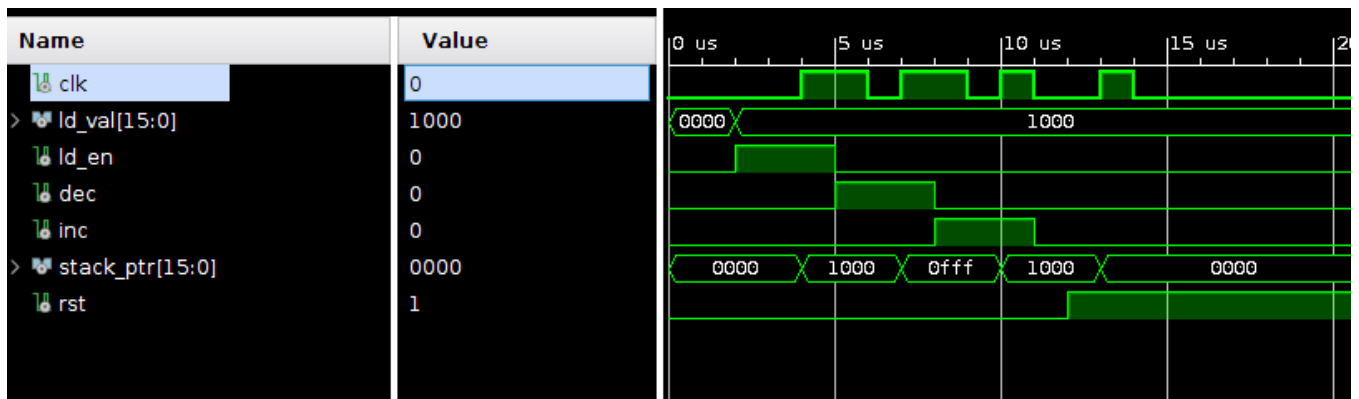


Figure 25: Stack Pointer Register